

1.

- a) Thévenin equivalent of right system: $V_{TH}=1$ p.u., $Z_{TH}=j0.15+j0.25=j0.4$ p.u.
 $S_{SC}=|V_{TH}|^2/Z_{TH}|=1/0.4=2.5$ p.u. or 2.5 p.u.*100MVA=**250 MVA**
- b) Consider one phase: Load current $I_{load}=1$ p.u. @ p.f. 1 = $1+j0$ p.u. Line-neutral voltage drop across Z_{TH} is $\Delta V=Z_{TH}I_{load}=j0.4*1$ p.u. With resistive load (p.f.=1), V_4 and ΔV differ by 90° so that $V_{TH}^2 = V_4^2 + (\Delta V)^2$. Magnitude of bus voltage $V_4=\sqrt{V_{TH}^2 - (\Delta V)^2} = \sqrt{1^2 - 0.4^2} = \mathbf{0.92 \text{ p.u.}}$
- c) Thévenin equivalent of left system seen from bus 2: $V_{TH}=1$ p.u., $Z_{TH}=(j0.1+j0.15)//(j0.2+j0.1)$ p.u.=0.136 p.u.
Thévenin equivalent of entire system seen from bus 4 after interconnection:
 $V_{TH}=1$ p.u., $Z_{TH}=(j0.136+j0.1)//(j0.15+j0.25)$ p.u.=0.149 p.u.
 $S_{SC}=|V_{TH}|^2/Z_{TH}|=1/0.149=6.73$ p.u. or 6.73 p.u.*100MVA=**673 MVA**
- d) Load current same as in 1b. Line-line voltage drop across Z_{TH} is $\Delta V=j0.149*1$ p.u. Magnitude of bus voltage $V_4=\sqrt{V_{TH}^2 - (\Delta V)^2} = \sqrt{1^2 - 0.149^2} = \mathbf{0.99 \text{ p.u.}}$

2.

- a) Voltage at both generator buses is 1 p.u. so $V_{TH}=1.0$ p.u. Z_{TH} is the impedance to ground from bus 3 with the (generator) voltage sources set to 0: $Z_{TH}=j0.2//j0.25=j0.11$ p.u. $S_{SC}=V_{TH}^2/Z_{TH}=9.0$ p.u. or **900 MVA**.
- b) $\partial V \approx -\partial Q/S_{SC}=-(50/100)/9.0$ p.u.=+0.056 p.u. The new voltage will be approximately $0.923+0.056$ p.u. =**0.979 p.u.**